

CSE 3203 CT 4 Assignment

Roll No: 1803109

Instruction: Covert this doc to PDF while uploading.

Assignment Problem:


Build CPU based on the following requirements:

1. Word Size of CPU = 5
2. ALU Operations = AND, ADD, SHR
3. Register Number = 4
4. Size of RAM = 7
5. Word size of ISA and RAM = 17
6. CPU Instructions = Register Mode, Immediate Mode, JMP, JG


Solution:

Simulator Design:

 
1. ALU Circuit (Top to Bottom all circuits):




Circuit: 5-Bit AND

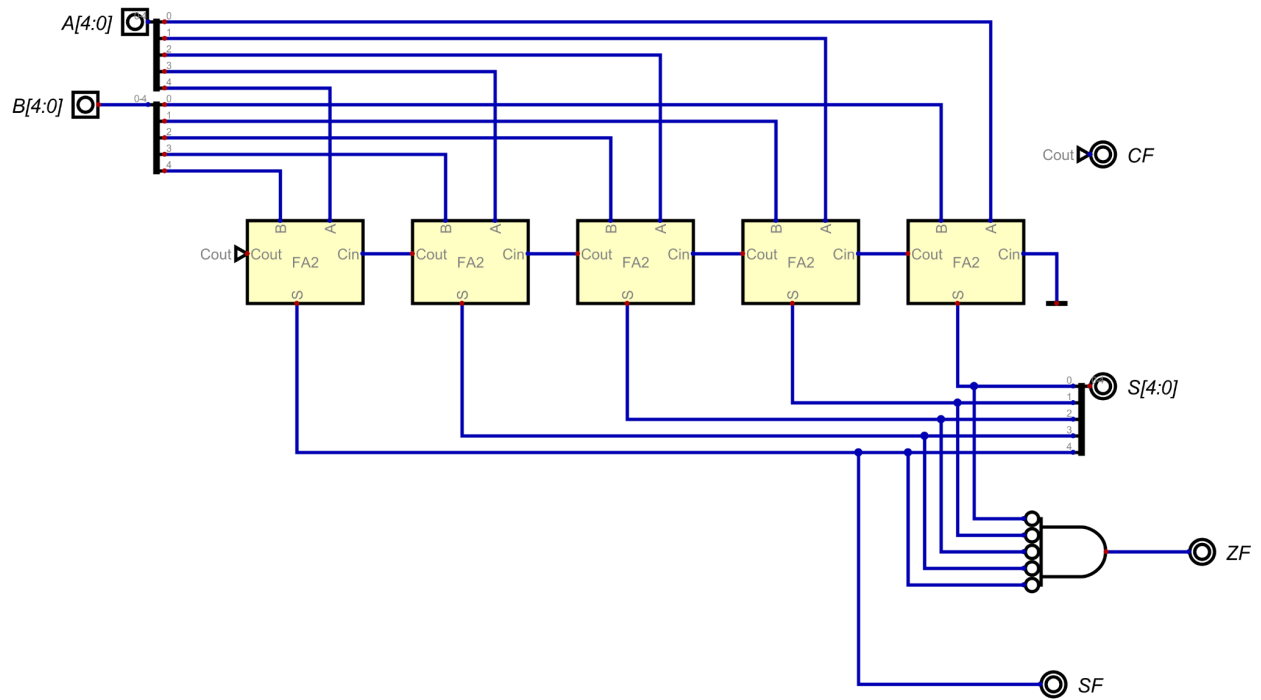

Circuit: 5-Bit ADD

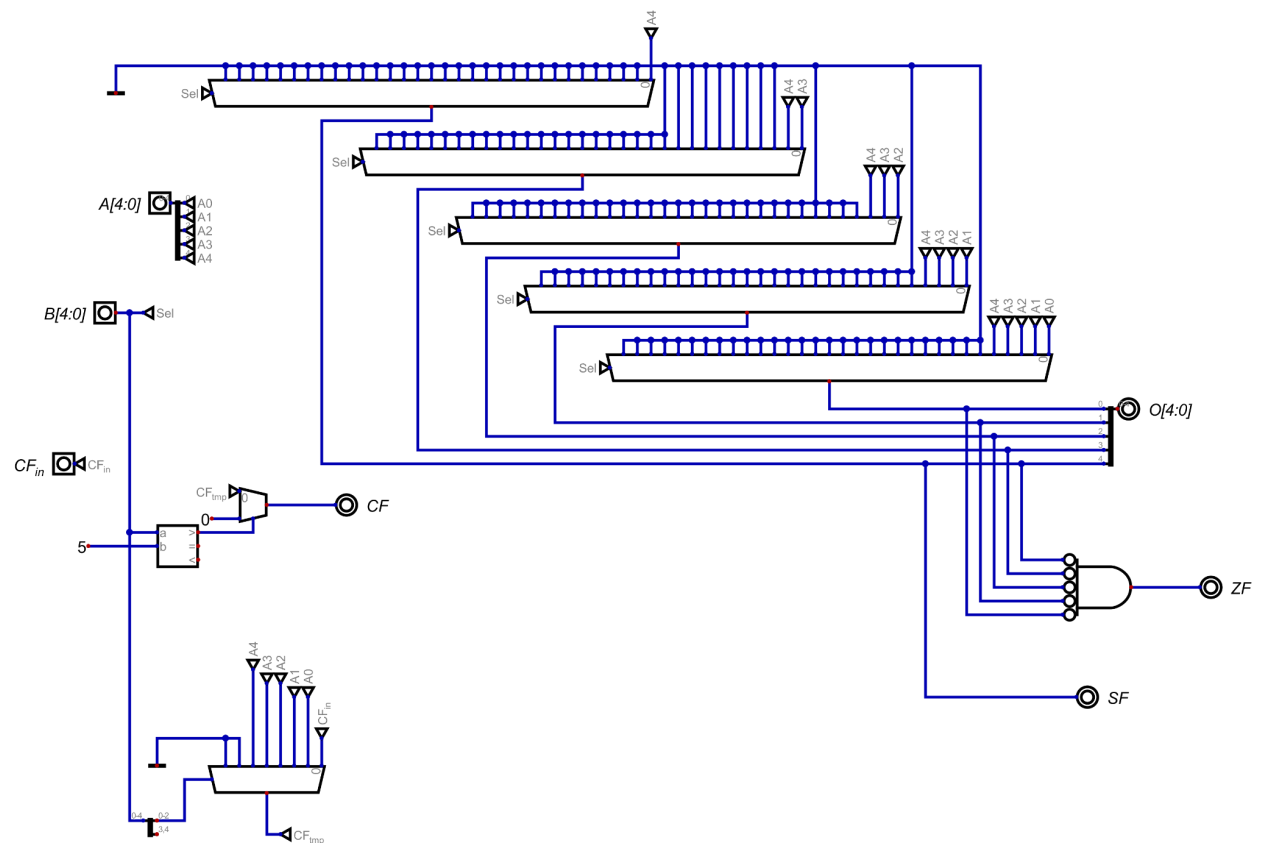


Circuit: 5-Bit SHR

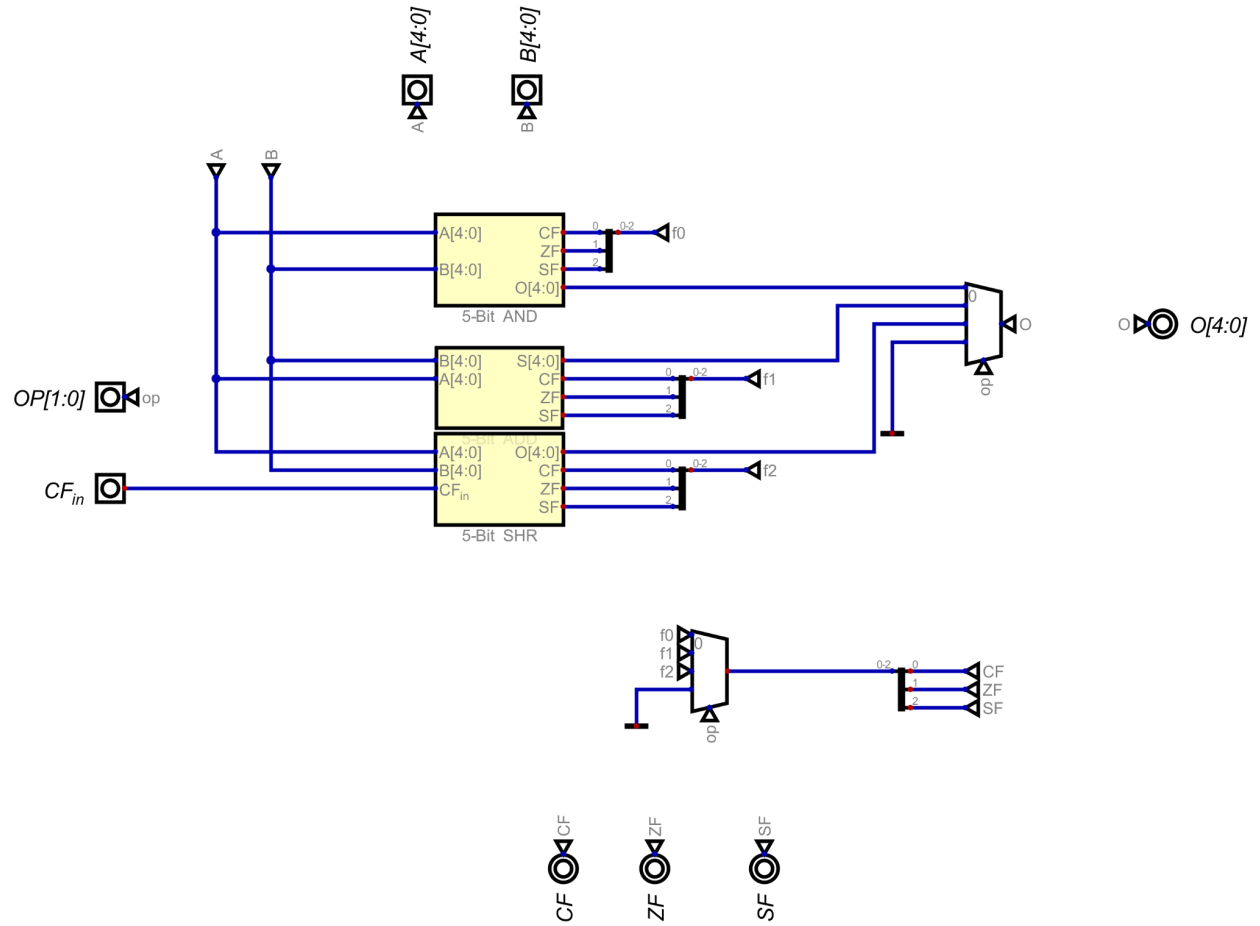


Circuit: 5 Bit ALU

 
2. Register Set Circuit (Top to Bottom all circuits):



Circuit: 1-Bit Register

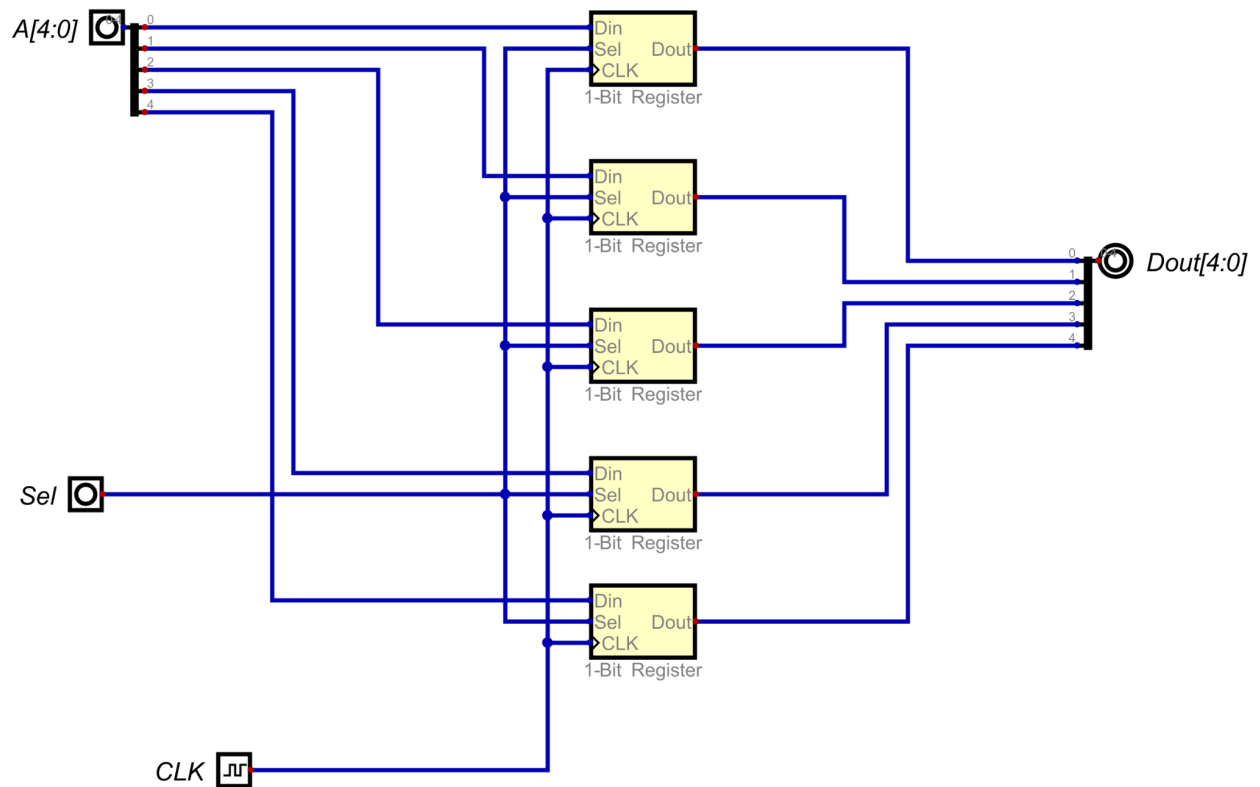


Circuit: 5-Bit Register

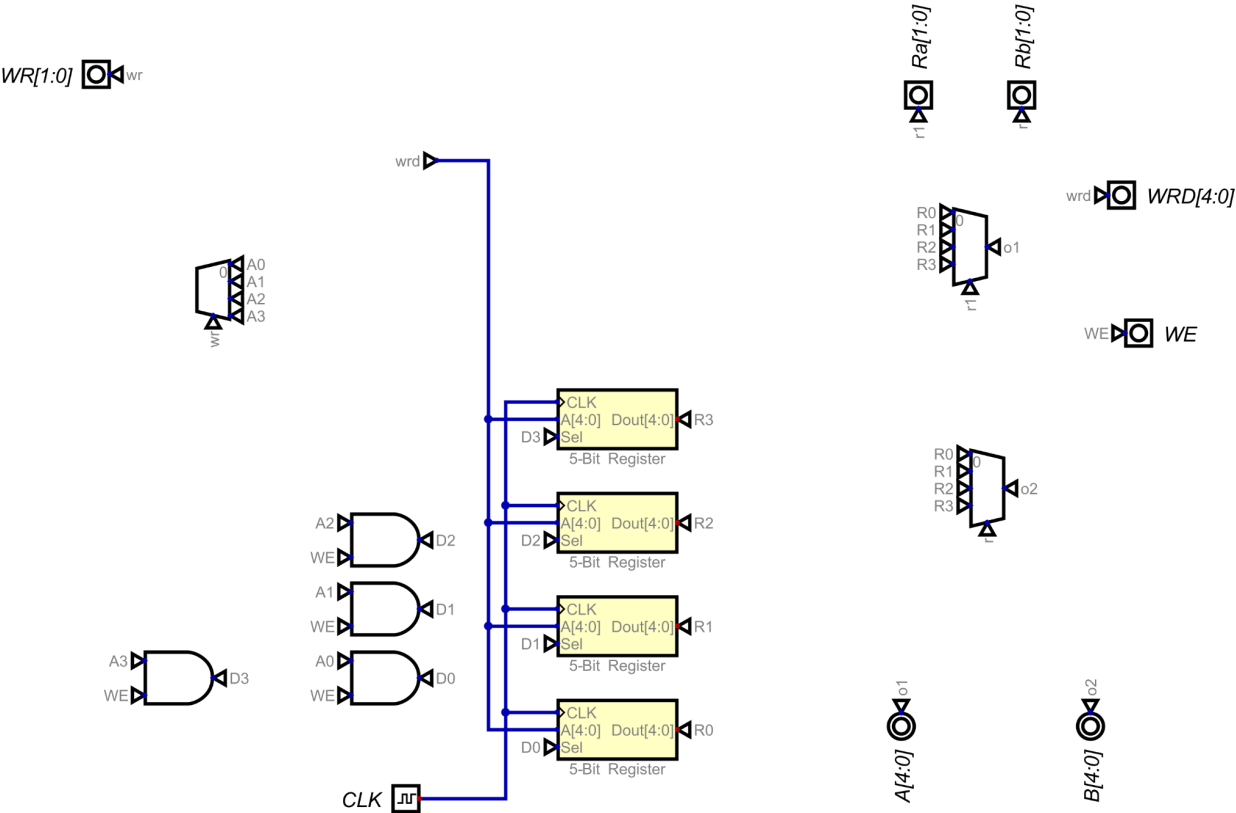


Circuit: 5-Bit Register Set with 4 Register

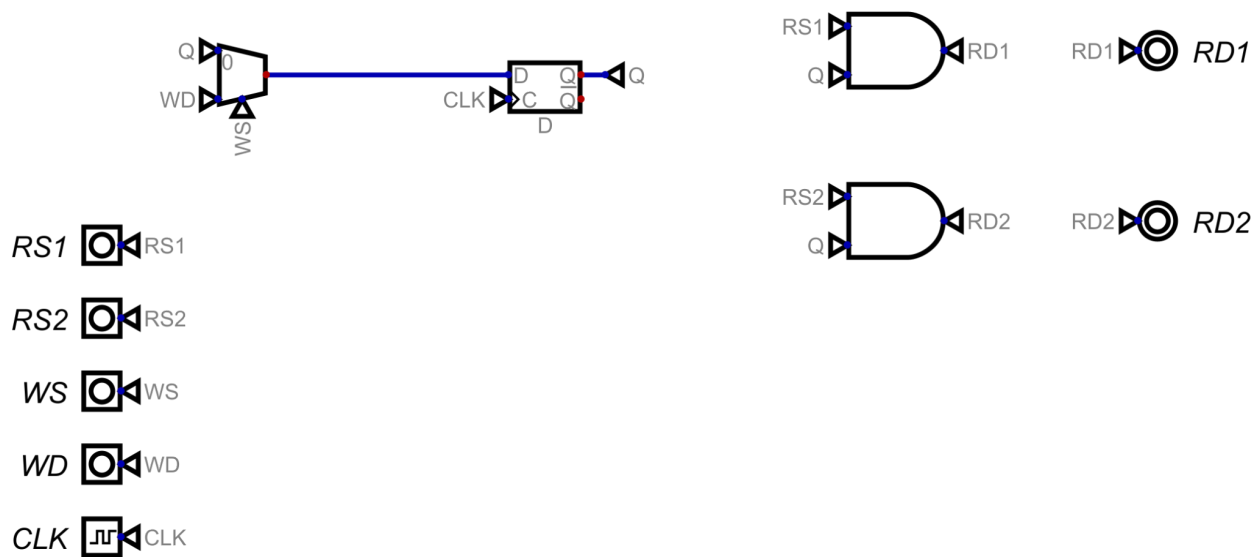
3. RAM Circuit (Top to Bottom all circuits):



Circuit: 1x1 RAM

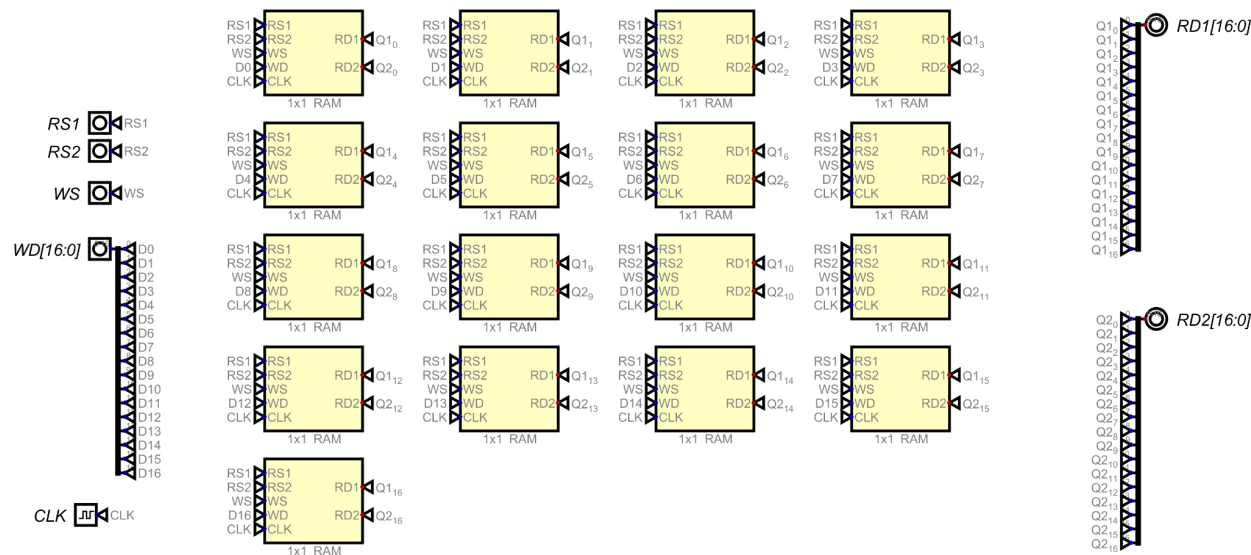

Circuit: 1x17 RAM

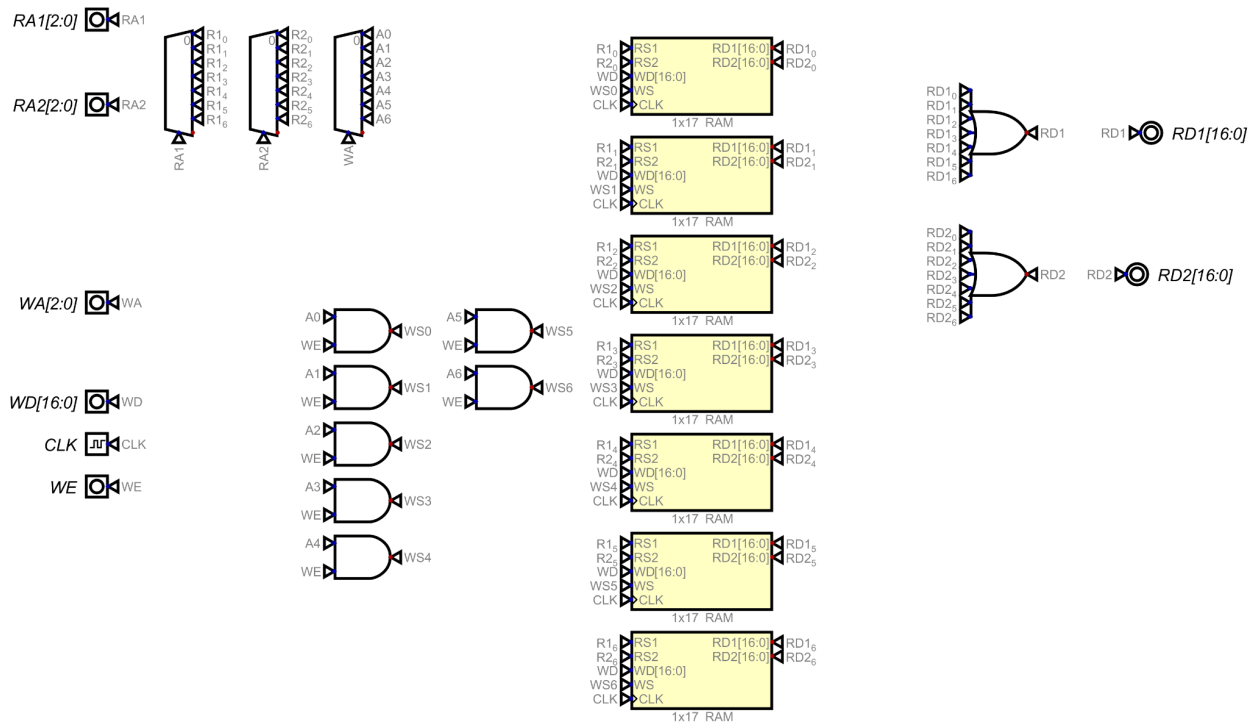

Circuit: 7x17 RAM

4. ISA

17 Bits ISA FOR ASSIGNED CPU

ISA of Register Mode:

Opcode(4 bits)		Register 1	Register 2	Unused
2 bits (16-15)	2 bit(14-13)	2 bits(12-11)	2 bits(10-9)	9 bits(8-0)
Types of operation(00)	Operations ALU selection line	Ra (00-11)	Rb (00-11)	X

Opcode(4 bits)		Register 1	Register 2	Unused
2 bits (16-15)	2 bit(14-13)	2 bits	2 bits	7 bits
00	00 (AND)	00-11	00-11	X
01	01 (ADD)	00-11	00-11	X
10	10(SHR)	00-11	00-11	X

ISA of Immediate Mode:


Opcode(4 bits)		Register 1	Constant	Unused
2 bits (16-15)	2 bit(14-13)	2 bits(12-11)	5 bits(10-6)	6 bits(5-0)
Types of operation (01)	Operations ALU selection line	Ra (00-11)	value (00000-11111)	X

Opcode(4 bits)		Register 1	Constant	Unused
2 bits (16-15)	2 bit(14-13)	2 bits	5 bits	6 bits
01	00(AND)	00-11	00000-11111	X
01	01 (ADD)	00-11	00000-11111	X
01	10(SHR)	00-11	00000-11111	X



ISA for Branching Mode:


Opcode(4 bits)		Address	Unused
2 bits (15-14)	2 bit(14-13)	3 bits(12-10)	10 bits(9-0)
Types of operation (10)	Operations ALU selection line	000-111 (RAM size=7)	X
10	00 (JMP)	000-111	X
10	01(JG)	000-111	X

5. CPU (Top to Bottom all circuits):

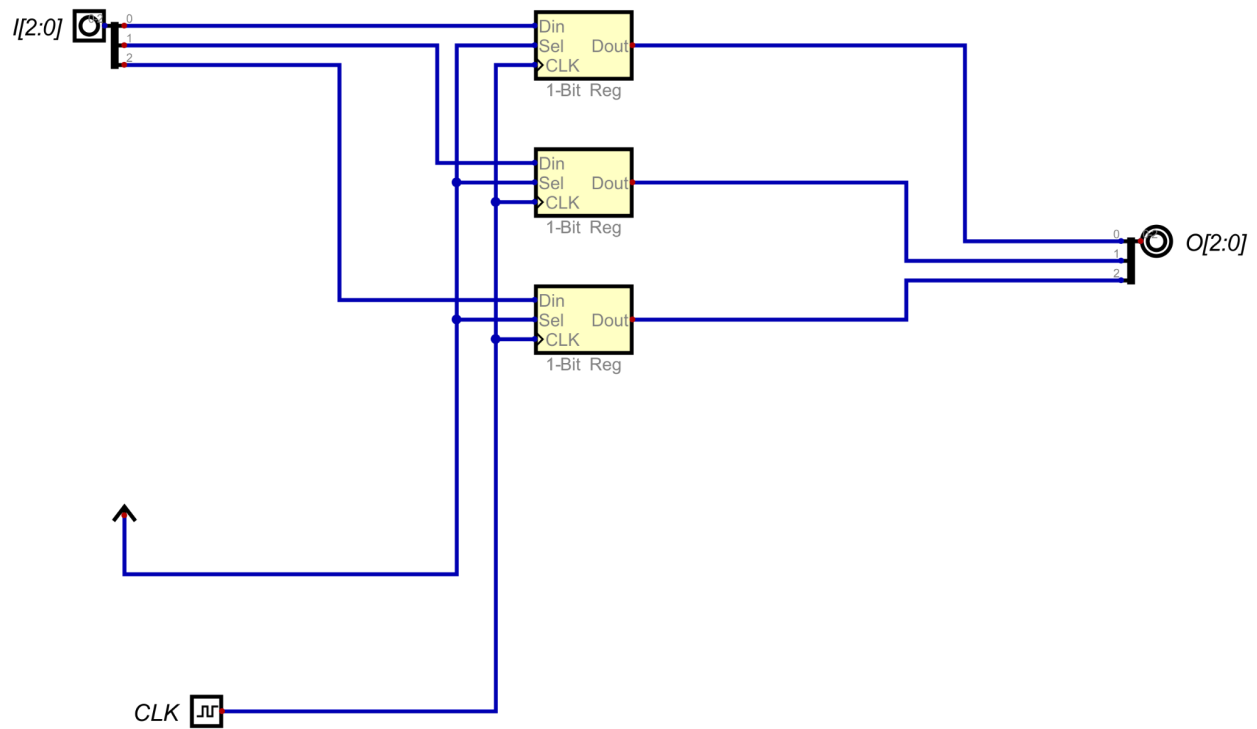

Circuit: 3-Bit Program Register

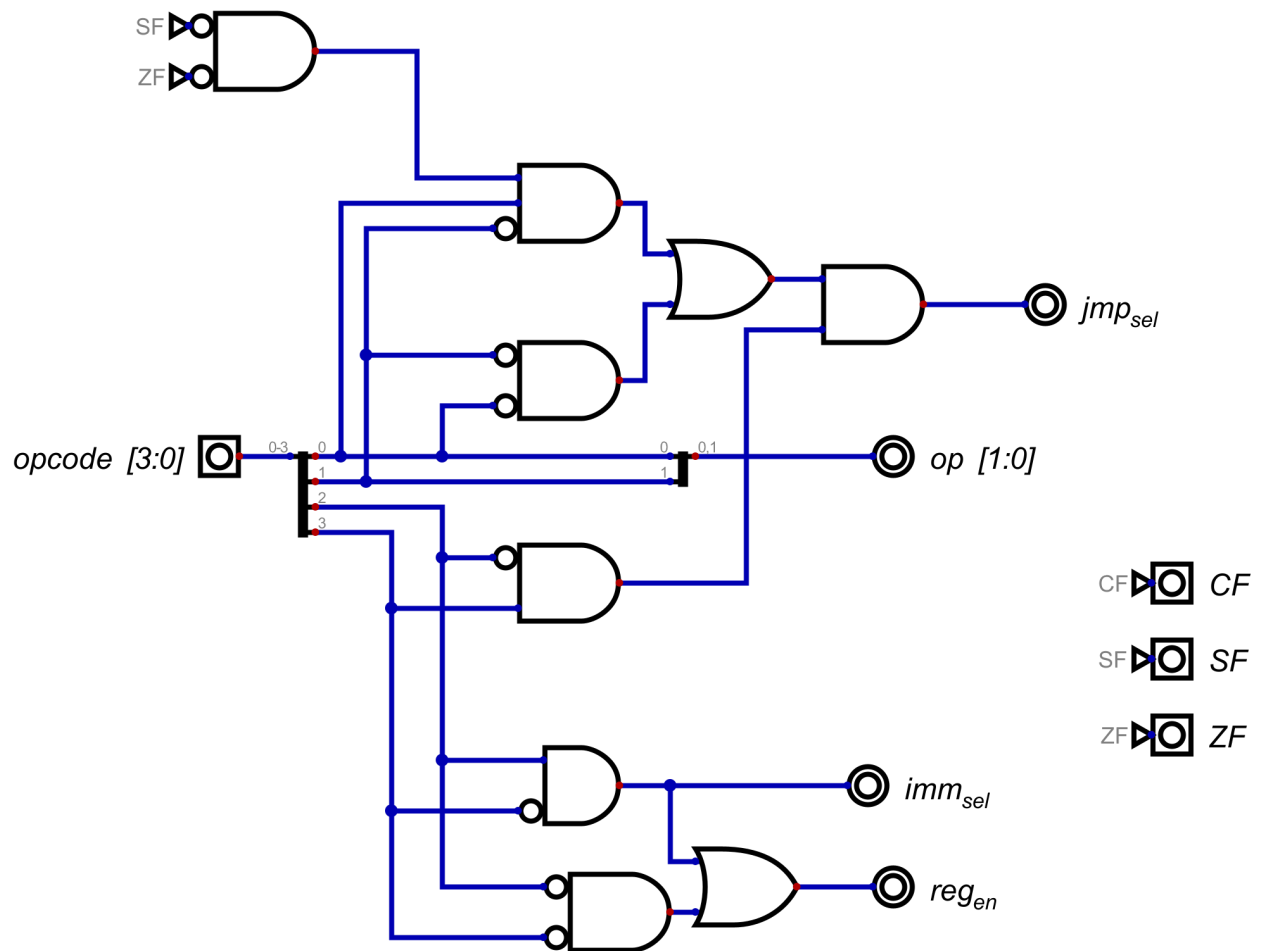 


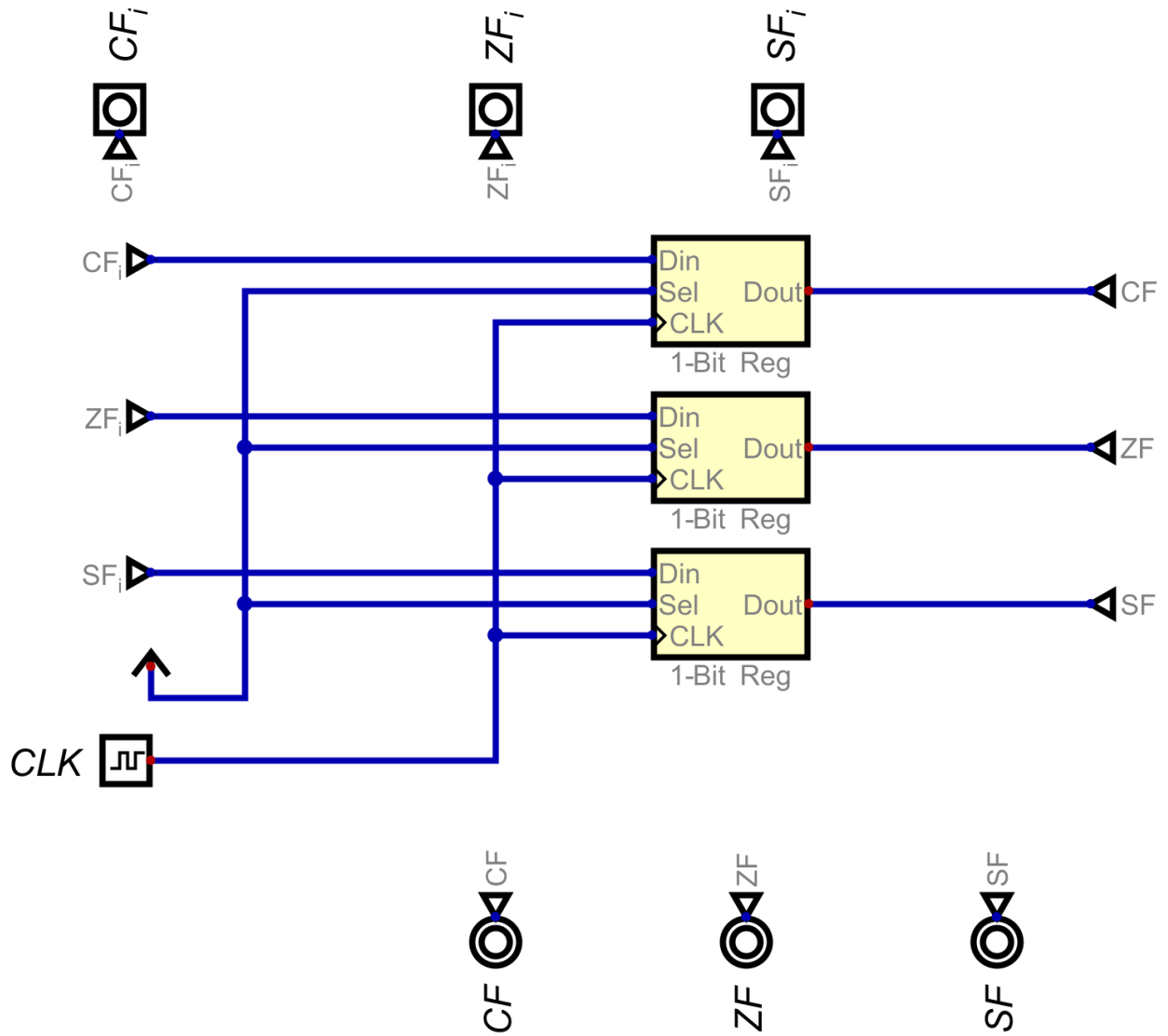

Circuit: Flag Register

Register Mode (Type of op=00)=2bit(Type of op)+ 2bit(no of op)+ 2bit(Reg1) + 2bit(Reg2) + 9bit(don't care)
 Immediate Mode (Type of op=01)=2bit(Type of op)+ 2bit(no of op)+ 2bit(Reg1) + 5bit(Imm value)+ 6 bit(dont' care)
 AND(op=00), ADD(op=01), SHR(op=10)
 JMP(op=00), JG(op=01)

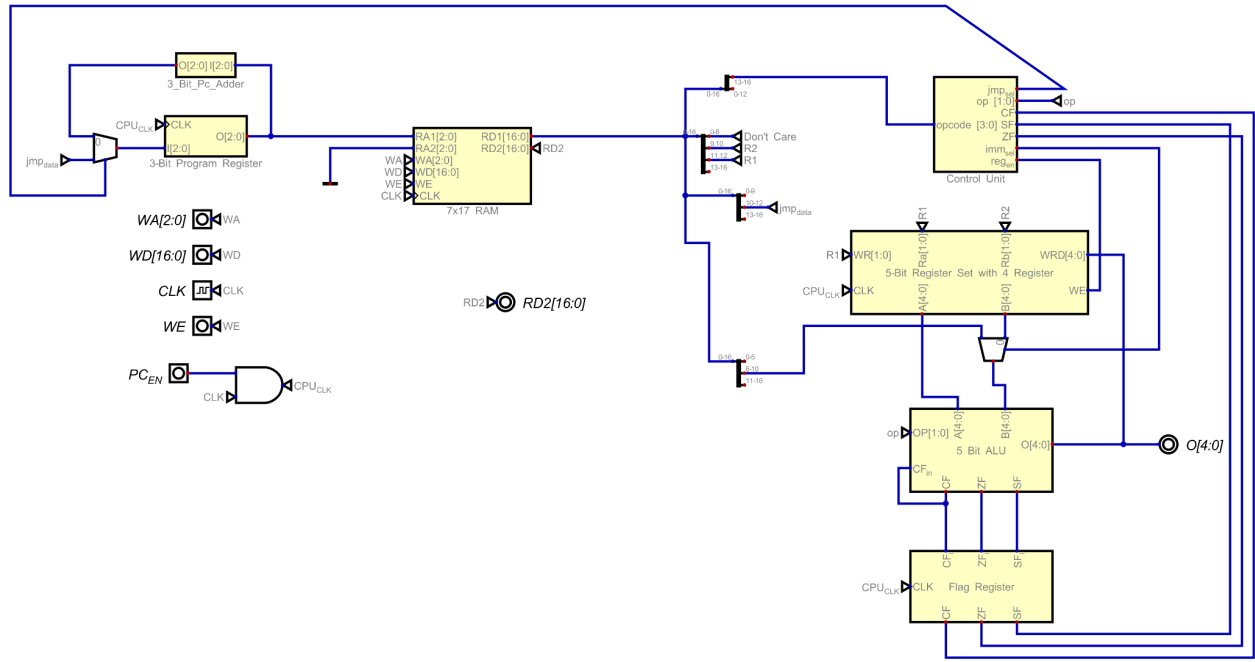AND R1,R1 -> 0000010100000000
 ADD R1,5 -> 0101010010100000
 ADD R2,4 -> 0101100010000000
 ADD R1,R2 -> 0001011000000000
 JMP 0 -> 1000000000000000
 SHR R1,4 -> 0110010010000000
 ADD R1,R1-> 0001010100000000



Circuit: 5_Bit_CPU

Verilog Code:

1. ALU Circuit (Top to Bottom all circuits):

and1bit.v

```
module and1bit(
    input a,
    input b,
    output r
);
    assign r=a&b;
endmodule
```

and1bit_tb.v

```
`timescale 1ns/1ps
module and1bit_tb;
    reg a;
    reg b;
    wire c;
    and1bit uut(.x(a), .y(b), .z(c));
    initial begin
        a = 0; b = 0; #10;
        a = 0; b = 1; #10;
        a = 1; b = 0; #10;
        a = 1; b = 1; #10;
        $finish;
    end
    initial begin
        $dumpfile("and1bit.vcd");
        $dumpvars(0, and1bit_tb);
        $monitor("a=%b    b=%b    c=%b", a,b,c);
    end
endmodule
```

and5bit.v

```
module and5bit(
    input wire [4:0] a,
    input wire [4:0] b,

    output wire [4:0] r,
    output wire cf,
    output wire zf,
    output wire sf
);
    and1bit uut0(
        .a(a[0]),
        .b(b[0]),
        .r(r[0])
    );
```

```

and1bit uut1(
    .a(a[1]),
    .b(b[1]),
    .r(r[1])
);

and1bit uut2(
    .a(a[2]),
    .b(b[2]),
    .r(r[2])
);

and1bit uut3(
    .a(a[3]),
    .b(b[3]),
    .r(r[3])
);

and1bit uut4(
    .a(a[4]),
    .b(b[4]),
    .r(r[4])
);

assign sf = r[4];
assign zf = (r == 5'b0);
assign cf = 1'b0;
endmodule

```

and5bit_tb.v

```

`timescale 1ns/1ps
module and5bit_tb;
    reg [4:0] a;
    reg [4:0] b;

    wire [4:0] r;
    wire cf;
    wire zf;
    wire sf;

    and5bit uut(a, b, r, cf, zf, sf);

```

```

    initial begin
        a <= 5'b10001;
        b <= 5'b00011;
        #20;
        a <= 5'b11111;
        b <= 5'b00001;
        #20;
        a <= 5'b11111;
        b <= 5'b10001;
        #20;
        $finish;
    end
    initial begin
        $dumpfile("and5bit.vcd");
        $dumpvars(0, and5bit_tb);

        $monitor("a=%b b=%b r=%b cf=%b sf=%b zf=%b", a, b, r,
cf, sf, zf);
    end
endmodule

```

add1bit.v

```

module add1bit(
    input wire A,
    input wire B,
    input wire Cin,
    output wire S,
    output wire Cout
);

assign S=A^B^Cin;
assign Cout=A&B | B&Cin |Cin&A;

endmodule

```

add1bit_tb.v

```
`timescale 1ns/1ps

module add1bit_tb;

    reg A;
    reg B;
    reg Cin;
    wire S;
    wire Cout;

    add1bit uut(
        .A(A) ,
        .B(B) ,
        .Cin(Cin) ,
        .S(S) ,
        .Cout(Cout)
    );

    initial begin

        $dumpfile("add1bit.vcd");
        $dumpvars(0,add1bit_tb);

        A=0;
        B=0;
        Cin=0;

        #20;
        B=1;

        #20;
        A=1;

        #20;
        B=0;

        #20;
        $finish;
    end
```



```

initial begin
    $monitor("A=%b B=%b Cin=%b | S=%b
Cout=%b\n",A,B,Cin,S,Cout);
end

endmodule

```

adder.v

```

module adder(
    input wire [4:0] a,
    input wire [4:0] b,

    output wire [4:0] s,
    output wire cf,
    output wire zf,
    output wire sf
);
    wire c1, c2, c3, c4;
    add1bit uut0(
        .A(a[0]),
        .B(b[0]),
        .Cin(1'b0),
        .S(s[0]),
        .Cout(c1)
    );
    add1bit uut1(
        .A(a[1]),
        .B(b[1]),
        .Cin(c1),
        .S(s[1]),
        .Cout(c2)
    );
    add1bit uut2(
        .A(a[2]),
        .B(b[2]),
        .Cin(c2),

```

```

        .S(s[2]),
        .Cout(c3)
    );
    add1bit uut3(
        .A(a[3]),
        .B(b[3]),
        .Cin(c3),
        .S(s[3]),
        .Cout(c4)
    );
    add1bit uut4(
        .A(a[4]),
        .B(b[4]),
        .Cin(c4),
        .S(s[4]),
        .Cout(cf)
    );
    assign sf = s[4];
    assign zf = (s == 5'b00000);
endmodule

```

adder_tb.v

```

`timescale 1ns/1ps
module adder_tb;
    reg [4:0] a;
    reg [4:0] b;

    wire [4:0] s;
    wire cf;
    wire zf;
    wire sf;

    adder uut(a, b, s, cf, zf, sf);

    initial begin
        a <= 5'b10001;
        b <= 5'b00011;
    end
endmodule

```

```

        #20;
        a <= 5'b11111;
        b <= 5'b00001;
        #20;
        $finish;

    end

    initial begin
        $dumpfile("adder.vcd");
        $dumpvars(0, adder_tb);

        $monitor("a=%b b=%b s=%b cf=%b sf=%b zf=%b", a, b, s,
cf, sf, zf);
    end
endmodule

```

shr5bit.v

```

module shr5bit(
    input [4:0] a,
    input [4:0] b,
    input cf0,
    output [4:0] r,
    output cf,
    output sf,
    output zf
);
    reg [4:0] res;
    always @(*) begin
        if (b == 0 )
            res <= a;
        else if (b == 1)
            res <= {1'b0, a[4:1]};
        else if (b == 2)
            res <= {2'b0, a[4:2]};
        else if (b == 3)
            res <= {3'b0, a[4:3]};
        else if (b == 4)
            res <= {4'b0, a[4]};
    end
endmodule

```

```

        else
            res <= 5'b0;
    end
    reg cf_tmp;
    always @(*) begin
        if (b == 0)
            cf_tmp <= cf0;
        else if (b == 1)
            cf_tmp <= a[0];
        else if (b == 2)
            cf_tmp <= a[1];
        else if (b == 3)
            cf_tmp <= a[2];
        else if (b == 4)
            cf_tmp <= a[3];
        else if (b == 5)
            cf_tmp <= a[4];
        else
            cf_tmp <= 1'b0;
    end
    assign r = res;

    assign cf = cf_tmp;
    assign sf = r[4];
    assign zf = (r == 5'b0);
endmodule

```

shr5bit_tb.v

```

`timescale 1ns/1ps
module shr5bit_tb;
    reg [4:0] a;
    reg [4:0] b;
    reg cf0;

    wire [4:0] r;
    wire cf;
    wire zf;

```

```

wire sf;

shr5bit uut(a, b, cf0, r, cf, zf, sf);

initial begin
    a <= 5'b11001;
    b <= 5'b00001;
    #20;
    a <= 5'b10011;
    b <= 5'b00100;
    #20;
    a <= 5'b11111;
    b <= 5'b00101;
    #20;
    $finish;
end
initial begin
    $dumpfile("shr5bit.vcd");
    $dumpvars(0, shr5bit_tb);

    $monitor("a=%b b=%b r=%b cf=%b sf=%b zf=%b", a, b, r,
cf, sf, zf);
end
endmodule

```

alu.v

```

module alu(
    input [4:0] a,
    input [4:0] b,
    input [1:0] op,
    input cf0,
    output [4:0] r,
    output cf,
    output sf,
    output zf
);
    wire [4:0] res0, res1, res2;

```

```

    wire [2:0] f0, f1, f2;

    and5bit uut0(.a(a), .b(b), .r(res0), .cf(f0[0]), .sf(f0[1]),
    .zf(f0[2]));

    adder uut1(.a(a), .b(b), .s(res1), .cf(f1[0]), .sf(f1[1]),
    .zf(f1[2]));

    shr5bit uut2(.a(a), .b(b), .cf0(cf0), .r(res2), .cf(f2[0]),
    .sf(f2[1]), .zf(f2[2]));

    reg [4:0] res;
    reg [2:0] f;
    always @(*) begin
        if (op == 0)
            begin
                res <= res0;
                f <= f0;
            end
        if (op == 1)
            begin
                res <= res1;
                f <= f1;
            end
        if (op == 2)
            begin
                res <= res2;
                f <= f2;
            end
        end
    end

    assign r = res;
    assign cf = f[0];
    assign sf = f[1];
    assign zf = f[2];

endmodule

```

alu_tb.v

```

`timescale 1ns/1ps
module alu_tb;
    reg [4:0] a;
    reg [4:0] b;
    reg [1:0] op;
    reg cf0;
    wire [4:0] r;
    wire cf;
    wire sf;
    wire zf;

    alu uut(a, b, op, cf0, r, cf, sf, zf);

    initial begin
        a <= 5'b00101;
        b <= 5'b00100;
        op <= 2'b01;
        #20;
        a <= 5'b10101;
        b <= 5'b01010;
        op <= 2'b00;
        #20;
        a <= 5'b10010;
        b <= 5'b00010;
        op <= 2'b10;
        #20;
        a <= 5'b11111;
        b <= 5'b00001;
        op <= 2'b01;
        #20;
        $finish;
    end
    initial begin
        $dumpfile("alu.vcd");
        $dumpvars(0, alu_tb);

        $monitor("op=%b a=%b b=%b cf0=%b r=%b  cf=%b sf=%b
zf=%b", op, a, b, cf0, r, cf, sf, zf);
    end
end

```

```
endmodule
```

Makefile

```
fa:
    iverilog -o add1bit.vvp add1bit.v add1bit_tb.v
    vvp add1bit.vvp
gtk_fa:
    gtkwave add1bit.vcd

adder: add1bit.v adder.v adder_tb.v
    iverilog -o adder.vvp add1bit.v adder.v adder_tb.v
    vvp adder.vvp

and: and1bit.v and5bit.v and5bit_tb.v
    iverilog -o and5bit.vvp and1bit.v and5bit.v and5bit_tb.v
    vvp and5bit.vvp

shr: shr5bit.v shr5bit_tb.v
    iverilog -o shr5bit.vvp shr5bit.v shr5bit_tb.v
    vvp shr5bit.vvp

alu: and1bit.v and5bit.v add1bit.v adder.v shr5bit.v alu.v
    alu_tb.v
    iverilog -o alu.vvp and1bit.v and5bit.v add1bit.v adder.v
    shr5bit.v alu.v alu_tb.v
    vvp alu.vvp

clear:
    rm -r *.vcd
    rm -r *.vvp
```

2. Register Set Circuit (Top to Bottom all circuits):

--

3. RAM Circuit (Top to Bottom all circuits):

--

4. CPU (Top to Bottom all circuits):

--